

## Scarica di un condensatore

$$\cancel{P} - Ri(t) - \frac{Q(t)}{C} = 0$$

$$-R \frac{dQ(t)}{dt} = \frac{Q(t)}{C}$$

$$-RC \frac{dQ(t)}{dt} = Q(t)$$

$$\frac{dQ(t)}{Q(t)} = - \frac{dt}{RC}$$

$$\int \frac{dQ(t)}{Q(t)} = - \int \frac{dt}{RC}$$

$$\ln Q(t) = - \frac{t}{RC} + K$$

$$-t/\tau + K$$

$$Q(t) = e$$

$$Q(0) = Q_0 = e^k$$

$$Q(t) = Q_0 e^{-t/\tau}$$

Energia solenoide

$$F = -L \frac{di}{dt}$$

$$dW = -dq \Delta V$$

$$dW = L \frac{di}{dt} dq = L \frac{dq}{dt} di$$

$$dW = L i di$$

$$\int_0^I dW = \int_0^I L i di$$

$$\int x dx = \frac{x^2}{2} + C$$

$$W = \left[ \frac{L i^2}{2} \right]_0^I = \frac{L I^2}{2}$$

$$\int_a^b f(x) dx = F(b) - F(a)$$

$$\int_0^{\pi} 3x^2 \cos x^3 dx = \left[ \sin x^3 \right]_0^{\pi} =$$
$$= \sin \pi^3 - \cancel{\sin 0} = \sin \pi^3$$

## Circuito RL

$$f - Ri - L \frac{di}{dt} = 0$$

$$f - Ri = L \frac{di}{dt}$$

$$\frac{dt}{L} = \frac{di}{f - Ri}$$

$$\int \frac{dt}{L} = -\frac{1}{R} \int \frac{f - Ri}{f - Ri} di$$

$$\ln(f - Ri) = -\frac{Rt}{L} + k$$

$$f - Ri = e^{-\frac{Rt}{L} + k}$$

$$Ri = \mathcal{E} - e^{-t/L + K}$$

$$i = \frac{\mathcal{E}}{R} - \frac{1}{R} e^{-t/L + K}$$

$$i(0) = 0 \quad \frac{\mathcal{E}}{R} - \frac{1}{R} e^K = 0$$

$$i = \frac{\mathcal{E}}{R} - \frac{\mathcal{E}}{R} e^{-t/L} = \frac{\mathcal{E}}{R} (1 - e^{-t/L})$$

Moti rettilineo

$$a = a(t)$$

MRUA

$$v(t) = \int a dt = at + c$$
$$v = at + v_0$$

$$s(t) = \int v(t) dt = \int (at + v_0) dt = \\ = \frac{1}{2} at^2 + v_0 t + \underbrace{k}_{s_0}$$

$$\mathcal{L} = \vec{F} \cdot \vec{s} \\ \vec{F} = -k\vec{x}$$

$$\mathcal{L} = \int kx dx = \frac{kx^2}{2} + C$$

$$\begin{aligned}
 \phi &= \int \left( k \frac{q_1 q_2}{r^2} dr = q_1 q_2 k \int \frac{1}{r^2} dr = \right. \\
 &= q_1 q_2 \frac{r^{-2+1}}{-2+1} + C = \\
 &= - \frac{q_1 q_2}{r} + C
 \end{aligned}$$

$$E = E_0 \sin(kx - \omega t)$$

$k = \frac{2\pi}{\lambda}$        $\omega = 2\pi f$

$$E(x, t) = E_0 \sin(kx - \omega t)$$

$$E_0 = 10 \text{ N/C}$$

$$f = 20 \text{ Hz}$$

$$E = E_0 \sin(kx - \omega t)$$

$$k = \frac{2\pi}{\lambda} \quad \omega = 2\pi f = 6,28 \cdot 20 = 124 \frac{\text{rad}}{\text{s}}$$

$$c = v = \frac{\lambda}{T} = \lambda f \quad \lambda = \frac{c}{f}$$

$$\lambda = \frac{3 \cdot 10^8}{2 \cdot 10} = 1,5 \cdot 10^7 \text{ m}$$

$$E = 10 \sin(4,18 \cdot 10^{-7} x - 124 t)$$