

Circuiti RC

Scarica

$$\cancel{V_0} - Ri(t) - \frac{q(t)}{C} = 0$$

$$-RC \frac{dq(t)}{dt} = q(t)$$

$$\frac{dq(t)}{q(t)} = - \frac{dt}{RC}$$

$$\int \frac{dq(t)}{q(t)} = - \int \frac{dt}{RC}$$

$$\ln q(t) = - \frac{t}{RC} + K \rightarrow \tau$$

$$q(t) = e^{-t/\tau + K}$$

$$q(0) = e^K = q_0$$

$$q(t) = e^{-t/\tau} \cdot q_0$$

$$i(t) = -q_0 \frac{1}{\tau} e^{-t/\tau} =$$

$$= -\frac{q_0}{RC} e^{-t/\tau} =$$

$$= -\frac{V_0}{R} e^{-t/\tau}$$

Energia imm. in solenoide

$$E = \frac{1}{2} L i^2$$

$$W = \vec{F} \cdot \vec{s}$$

$$W = \int F \cdot ds$$

$$dW = -dq \quad V = -dq \left(-L \frac{di}{dt} \right) =$$

$$= L \frac{dq}{dt} di = L i di$$

$$\int_0^{\bar{I}} dW = \int_0^{\bar{I}} L i di$$

$$W = L \left[\frac{i^2}{2} \right]_0^{\bar{I}} = L \frac{\bar{I}^2}{2}$$

Circuito RL

chiusura

$$V_0 - Ri - L \frac{di}{dt} = 0$$

$$V_0 - Ri = L \frac{di}{dt}$$

$$\frac{di}{V_0 - Ri} = \frac{dt}{L}$$

$$\int \frac{-R di}{V_0 - Ri} = \int \frac{dt}{L}$$

$$-\frac{1}{R} \ln(V_0 - Ri) = t/L$$

$$\ln(V_0 - Ri) = -\frac{R}{L} t + k$$

$$V_0 - Ri = e^{-t/\tau} + k$$

$$i = \frac{V_0 - e^{-t/\tau} + k}{R}$$

$$i(0) = \frac{V_0 - e^k}{R} = 0$$

$$e^k = V_0$$

$$i(t) = \frac{V_0}{R} - \frac{V_0}{R} e^{-t/\tau} =$$

$$= \frac{V_0}{R} (1 - e^{-t/\tau})$$

Apertura

$$-Ri - L \frac{di}{dt} =$$

$$-Ri = L \frac{di}{dt}$$

$$-\frac{di}{Ri} = \frac{dt}{L}$$

$$\frac{di}{i} = -\frac{R}{L} dt$$

$$\int \frac{di}{i} = -\frac{R}{L} \int dt$$

$$\ln i(t) = -\frac{R}{L} t + k$$

$$i(t) = e^{-t/\tau + k}$$

$$i(0) = e^k = I_0$$

$$i(t) = I_0 e^{-t/\tau}$$

$$\int \frac{f'(x)}{f(x)} dx = \ln |f(x)| + k$$